
SAMA5D2 Hardware Design Considerations

Scope

This document facilitates the bring-up of any hardware design featuring a SAMA5D2 MPU by providing a short checklist for the hardware designer.

Abbreviations

- SDRAM – Synchronous Dynamic Random Access Memory
- DDR – Double Data Rate
- LP – Low Power
- PCB – Printed Circuit Board

Reference Documents

All the documents listed below are available on www.microchip.com.

Type	Name
Data sheet	SAMA5D2 Series
Data sheet	SAMA5D29
Errata	SAMA5D2 Device Silicon Errata and Data Sheet Clarification
Errata	SAMA5D29 Device Silicon Errata and Data Sheet Clarification
Board design files	ATSAMA5D2C-XULT board design files

Table of Contents

Scope.....	1
Abbreviations.....	1
Reference Documents.....	1
1. Design Checklists.....	3
1.1. Schematic Checklist.....	3
1.2. Layout Checklist.....	3
2. Schematic Checklist Description and Examples.....	4
2.1. Provide Adequate Voltage and Sufficient Current.....	4
2.2. Ensure Correct Power-Up and Power-Down Sequences.....	5
2.3. Ensure that the Power Supply Pins have Adequate Decoupling Capacitors.....	6
2.4. Check MPU Configuration.....	7
2.5. Check the DDR Controller Configuration.....	8
3. Layout Checklist Description and Examples.....	14
3.1. Check that the Board has an Uninterrupted GND Plane.....	14
3.2. Define a Layer Stack-Up so that Line Impedances are matched to Driver Impedances.....	15
3.3. Place Decoupling Capacitors as Close as Possible to IC Pins.....	19
3.4. Length-Match High-Speed Signals.....	21
4. Revision History.....	24
4.1. Rev. A - 03/2022.....	24
5. Appendix.....	25
5.1. Bit and Byte Swapping.....	25
5.2. Good Practices.....	26
The Microchip Website.....	27
Product Change Notification Service.....	27
Customer Support.....	27
Microchip Devices Code Protection Feature.....	27
Legal Notice.....	27
Trademarks.....	28
Quality Management System.....	29
Worldwide Sales and Service.....	30

1. Design Checklists

1.1 Schematic Checklist

- Is the MPU supplied with the correct voltage levels?
- Does the power management IC provide enough current for the system?
- Are the correct power supply power-up and power-down sequences implemented?
- Are the decoupling capacitors adequate?
- Is the MPU configured correctly?
- Is the DDR controller configured correctly?

1.2 Layout Checklist

- Does the board feature an uninterrupted GND plane?
- Is a proper layer stack-up defined?
- Are the decoupling capacitors placed as close as possible to the IC pins?
- Are high-speed signal lengths matched and routed over continuous planes (USB, SDCARD, DDR, etc.)?

2. Schematic Checklist Description and Examples

This section describes each item in the schematic checklist and provides implementation examples.

2.1 Provide Adequate Voltage and Sufficient Current


2.1.1 Requirements

Refer to table “SAMA5D2 Power Supplies”, in section “Power Considerations” of the SAMA5D2 data sheet, for the power supplies needed to power the MPU.

2.1.2 Implementation Example

The MCP16502 and MCP16501 PMICs are designed especially for SAMA5D2 applications, as they can output all the power supply domains required by the MPU.

Figure 2-1. Application Schematic Example with MCP16502AA

 

2.2.1 Requirements

The table “Power-up Timing Specification” establishes that:

- The table “Power-down Timing Specification” establishes that:

- All these power-up and power-down requirements are already implemented in the MCP16502/1 PMIC solutions.

2.3 Ensure that the Power Supply Pins have Adequate Decoupling Capacitors

2.3.1 Requirements


Low-impedance decoupling/filtering of the device power supply inputs must be provided. A 100 nF ceramic X7R (or X5R) capacitor placed very close to each power supply input is a minimum requirement. A 10 μ F ceramic X7R (or X5R) ceramic capacitor should also be placed on the VDDCORE and VDDIODDR power rails, close to the MPU.

In the SAMA5D2-XULT, we have opted for 100 nF 0402, X7R rated at 16V and 10 μ F 0805, X5R rated at 16V multilayer ceramic capacitors with good results. Smaller sized capacitors provide better decoupling due to reduced inductance.

2.3.2 Implementation Example

It is recommended to separate the power inputs of the internal oscillators and PLL circuits (VDDOSC, VDDAUDIOPLL and VDDPLLA) using a series 10 μ H inductors on each input. Other peripheral power inputs (VDDIOP0, VDDIOP1, VDDISC etc.) may use series 180 Ω ferrite beads instead when necessary, but the preferred choice is to connect those belonging to the same voltage in a single, solid, unsplit power plane..

Figure 2-3. Processor Power Supplies

 

2.4 Check MPU Configuration

2.4.1 Requirements

- A 5.62 k Ω resistor is connected to the VBG pin for USB external tuning and an adequate voltage divider is placed on USB VBUS to transform the 5V into the PIO voltage.
Refer to “Typical Connection” in sections “USB High Speed Device Port (UDPHS)” and “USB Host High Speed Port (UHPHS)” of the SAMA5D2 data sheet.
- The TST pin is grounded.
- If the design does not need JTAG boundary scan, tie the JTAGSEL pin to GND or leave it floating.
- The SDCAL calibration cell input should be connected to ground with a 20 k Ω resistor for 1.8V SDMMC memories or a 16.9 k Ω resistor for 3.3V memories. If the memory device operates in both 1.8V and 3.3V modes, then use a 20 k Ω resistor.
- A 32.768 kHz crystal is placed between XIN32 and XOUT32.
Refer to section “32.768 kHz Crystal Oscillator Characteristics” in the “Electrical Characteristics” of the SAMA5D2 data sheet.
- A high-frequency clock source is provided either through a crystal oscillator placed between XIN and XOUT or through an external clock generator.
Refer to section “Main Oscillator Characteristics” in the “Electrical Characteristics” of the SAMA5D2 data sheet.
- If the clock generator option is chosen, it is recommended to ground XOUT to improve stability.
- Clock sources should be chosen with great care.
Refer to section “Recommended Crystal Characteristics” in the “Electrical Characteristics” of the SAMA5D2 data sheet.

2.4.2 Implementation Example

Figure 2-4. Main Oscillator Connection



 


Figure 2-5. 32 kHz Oscillator Connection

 

In the design schematic below, the SAMA5D2 MPU features the 12MHz DSC1001DL5-012.0000 MEMS oscillator as default main clock source and the NX2012SA-32.768K-STD-MUB-1 crystal loaded with 18 pF capacitors to provide the 32.768 kHz slow clock. Alternatively, by removing R1 and R2 resistors and populating the corresponding parts associated with Y2, then the CX3225SB12000H0PSTC1 12MHz crystal oscillator is used as main clock source.

Figure 2-6. Processor Configuration

 

2.5 Check the DDR Controller Configuration


2.5.1 Requirements

- Connect the external memory chosen as required in table "I/O Lines Usage vs. Operating Mode" in the section "External Memories" of the SAMA5D2 data sheet.
- Select the correct value for DDR_CAL depending on the memory used:
 - 21 kΩ for DDR2 and LPDDR1
 - 22 kΩ for DDR3
 - 23 kΩ for DDR3L
 - 24 kΩ for LPDDR2/LPDDR3
- Connect the DDR_VREF pin to VDDIOM/2
- SiP (System-in-Package) versions of the SAMA5D2 MPUs do not have a DDR_CAL pin. They do feature the ZQ pin necessary for the embedded DRAM, which should be connected to ground with a 240Ω resistor.

Refer to “DDR I/O Calibration” in the section “Memories” of the SAMA5D2 data sheet.

2.5.2 Implementation Example for 16-bit DDR2

Figure 2-7. 16-bit DDR2 Hardware Configuration

 

2.5.3 Implementation Example for 2x16-bit DDR2

Figure 2-8. 2x16-bit DDR2 Hardware Configuration


 


Figure 2-11. 2x16-bit LPDDR2 Hardware Configuration

 

3. Layout Checklist Description and Examples

3.1 Check that the Board has an Uninterrupted GND Plane

3.1.1 Requirements

A PCB with a low-impedance ground plane must be provided. A single unbroken ground plane is a minimum requirement.

3.1.2 Implementation Example

[Figure 3-1](#) depicts a solid/uninterrupted GND plane that stretches all over the board. This is the ideal implementation.

[Figure 3-2](#) shows several cut-outs assigned to a different power supply. This arrangement is to be avoided by all means, as it is a proven source of EMI, therefore prone to failing the EMC compliance tests.

Figure 3-1. Correct GND Plane


 


Figure 3-2. Incorrect GND Plane

 

3.2 Define a Layer Stack-Up so that Line Impedances are matched to Driver Impedances

3.2.1 Requirements

Match the PCB line impedances to their corresponding driver impedances to reduce line reflections:

- Single-ended lines should have $50\Omega \pm 10\%$ single-ended impedance.
- USB lines should have $90\Omega \pm 15\%$ differential impedance.
- DDR CLOCK and STROBE should have $100\Omega \pm 10\%$ differential impedance.

3.2.2 Implementation Example

The SAMA5D2 is available in multiple packages of different sizes and requirements:

Package Name	Pin Count	Ball Pitch
LFBGA289	289	0.8 mm
TFBGA256	256	0.4 mm
TFBGA196	196	0.75 mm

Layout Checklist Description and Examples

To optimize performance, we recommend using the layer stack-ups, line widths and clearances in the following illustrations.

These stack-ups were selected because they can provide all the required impedances by using minimum 100 μm -wide traces.

The minimum trace width is 100 μm (~4 mil) which is standard for PCB manufacturers. This also ensures that the routing does not take much space on the board.

SAMA5D2 MPUs available in a TFBGA196 package can be implemented on a PCB with a stack-up of minimum four layers.

Figure 3-3. 4-Layer Stack-Up

4-Layer Stack Legend

Material	Layer	Thickness	Dielectric	Material	Type	Gerber
	Top Overlay				Legend	GTO
	Surface Material	Top Solder	0.020mm	Solder Resist	Solder Mask	GTS
Copper	L1 - Top Layer	0.035mm			Signal	GTL
Prepreg		0.085mm			Dielectric	
Copper	L2 - GND	0.035mm			Signal	G1
Core		1.200mm	FR-4		Dielectric	
Copper	L3 - PWR	0.035mm			Signal	G2
Prepreg		0.085mm			Dielectric	
Copper	L4 - Bottom Layer	0.035mm			Signal	GBL
	Surface Material	Bottom Solder	0.020mm	Solder Resist	Solder Mask	GBS
	Bottom Overlay				Legend	GBO
Total thickness: 1.560 mm $\pm$ 10%						

PCB Impedance Information

TYPE	IMPEDANCE	TOLERANCE	LAYER	REFERENCE	WIDTH [μm]	GAP [μm]
DIFF	90 Ω	$\pm$ 10%	L1	L2	125	200
DIFF	90 Ω	$\pm$ 10%	L4	L3	125	200
DIFF	100 Ω	$\pm$ 10%	L1	L2	100	200
DIFF	100 Ω	$\pm$ 10%	L4	L3	100	200
SE	50 Ω	$\pm$ 10%	L1	L2	125	
SE	50 Ω	$\pm$ 10%	L4	L3	125	

SAMA5D2 MPUs available in TFBGA289 package can be implemented on a PCB with a stack-up of minimum six layers.

Figure 3-4. 6-Layer Stack-Up

6-Layer Stack Legend


	Material	Layer	Thickness	Dielectric Material	Type	Gerber
		Top Overlay			Legend	GTO
	Surface Material	Top Solder	0.025mm	Solder Resist	Solder Mask	GTS
	Copper	L1 - Top	0.035mm		Signal	GTL
	Prepreg		0.085mm		Dielectric	
	Copper	L2 - GND	0.035mm		Signal	G1
	Core		0.100mm	FR-4	Dielectric	
	Copper	L3 - Signal	0.035mm		Signal	G2
	Prepreg		0.950mm		Dielectric	
	Copper	L4 - Signal	0.035mm		Signal	G3
	Core		0.100mm	FR-4	Dielectric	
	Copper	L5 - PWR	0.035mm		Signal	G4
	Prepreg		0.085mm		Dielectric	
	Copper	L6 - Bottom	0.035mm		Signal	GBL
	Surface Material	Bottom Solder	0.025mm	Solder Resist	Solder Mask	GBS
		Bottom Overlay			Legend	GBO
Total thickness: 1.60 mm $\pm$ 10%						

PCB Impedance Information

TYPE	IMPEDANCE	TOLERANCE	LAYER	REFERENCE	WIDTH [um]	GAP [um]
DIFF	90Ω	$\pm$ 10%	L1	L2	125	200
DIFF	90Ω	$\pm$ 10%	L6	L5	125	200
DIFF	100Ω	$\pm$ 10%	L1	L2	100	200
DIFF	100Ω	$\pm$ 10%	L6	L5	100	200
SE	50Ω	$\pm$ 10%	L1	L2	125	
SE	50Ω	$\pm$ 10%	L6	L5	125	
SE	50Ω	$\pm$ 10%	L3	L2	125	
SE	50Ω	$\pm$ 10%	L4	L5	125	

SAMA5D2 MPUs available in TFBGA256 package can be implemented on a PCB with a stack-up of minimum eight layers.

Figure 3-5. 8-Layer Stack-Up

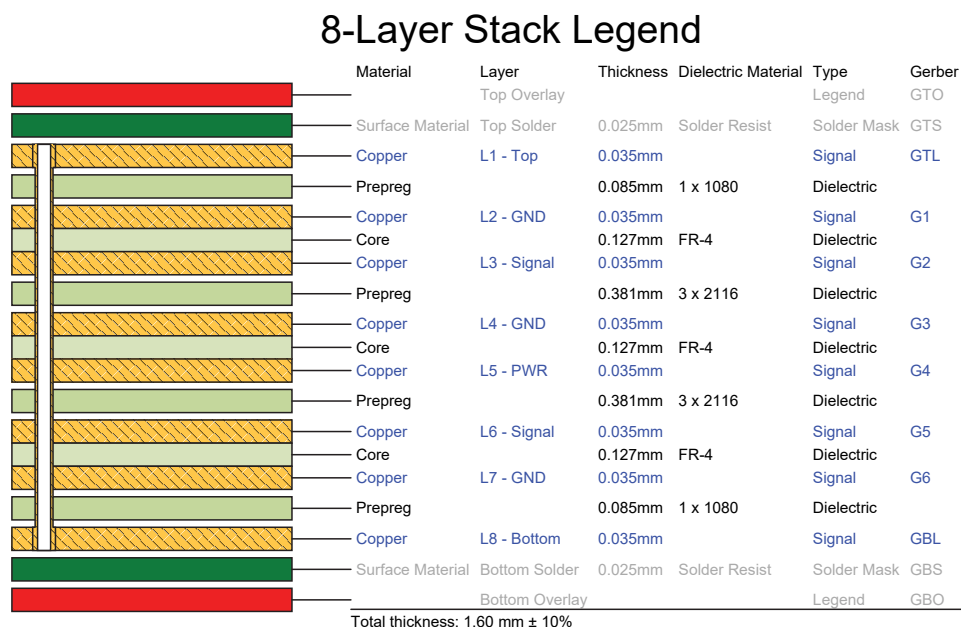

PCB Impedance Information

TYPE	IMPEDANCE	TOLERANCE	LAYER	REFERENCE	WIDTH [um]	GAP [um]
DIFF	90Ω	± 10%	L1	L2	125	200
DIFF	90Ω	± 10%	L8	L7	125	200
DIFF	100Ω	± 10%	L1	L2	100	200
DIFF	100Ω	± 10%	L8	L7	100	200
SE	50Ω	± 10%	L1	L2	125	
SE	50Ω	± 10%	L8	L7	125	
SE	50Ω	± 10%	L3	L2;L4	125	
SE	50Ω	± 10%	L6	L5;L7	125	

3.2.3 Additional Tips



Important: Ensure that your PCB manufacturer can produce the specific stack-up.

If the PCB manufacturer does not have the required materials in stock and has to order them specifically, overall production costs may be increased.


Additionally, the manufacturer may recommend a different layer stack-up that can be produced at a lower cost with the materials in stock.

In such cases, a layout can be easily adapted to the recommended stack-up by changing the width of the traces so the required impedances are preserved. With the help of an impedance calculator tool, ensure that the recommendations given in this document are respected (e.g. check that enlarging the traces satisfies the impedance while not infringing the minimal spacing).

Using an impedance calculator eases the design of proper transmission lines. The following example shows the Altium Designer impedance calculator.

After defining the PCB stack-up, you can either use the software to compute the ideal trace width that will yield a specific impedance, or input the trace width so that the tool calculates the resulting impedance.

Figure 3-6. Impedance Calculation

 

The ATSAMA5D2C-XULT was designed on a six-layer PCB so that the final thickness of the board should be 1.6 mm. Designs which require a different board thickness can be obtained only by modifying the central dielectric height. This does not impact the previously calculated trace impedances.

3.3 Place Decoupling Capacitors as Close as Possible to IC Pins

3.3.1 Requirements

Low-impedance decoupling of the device power supply inputs must be provided. The minimum requirement is that of 100nF ceramic X7R (or X5R) capacitors are placed very close to each power supply input.

3.3.2 Implementation Example

The SAMA5D2 BGA289 is a full 17x17 ball grid array without any depopulated balls. In order to fit 0402 decoupling capacitors on each pin, the capacitor pads land on vias used to connect to power planes, therefore the PCB should be manufactured in respect of this constraint.

Using 0201 decoupling capacitors eliminates the via-in-pad constraint and are the preferred option due to their better performance.

Power is supplied through solid copper polygons placed on the inner layer (power layer). These polygons are formed in such a way that the signals on the bottom layer have their return path through them.

In the ATSAMA5D2C-XULT design files, the power planes are split to allow the user to measure the MPU power consumption, which was a requirement of the evaluation board. However, if this is not a requirement in your design, we highly recommend a single unsplit plane for each power rail.

In the following figure, capacitors are the green rectangles.

Figure 3-7. SAMA5D2 BGA289 Capacitor Placement


 


Figure 3-8. SAMA5D2 BGA289 Power Planes

 

3.4 Length-Match High-Speed Signals

3.4.1 Requirements

High-speed signals must be length-matched and routed over an uninterrupted reference plane (power or ground).

3.4.2 Implementation Example

When routing a 32-bit bus width DRAM interface, it is recommended to use 2x16-bit memory devices. The two devices should be routed using a tree topology, with a midpoint split for the address/command/control signals bus.

For this bus, length matching should be done so that traces connecting the individual memory device to the MPU are matched within a margin.

Traces from each data byte lane should also be matched within its own lane.

It is good practice to route data signals that belong to the same byte lane on the same layer. [Figure 3-10](#) shows the signal routing of data byte lane 0 and 2. For the address/command/control signals bus in [Figure 3-9](#), the routing constraints can be relaxed and routing can be made on any available signal layer.

It is recommended to route the DRAM clock and DQS differential signals on the top and bottom layer, or on the same layer as the rest of the signals from the same group.

Figure 3-9. DDR3L Address and Control


 


Figure 3-10. DDR3L Data Lanes

 

4. Revision History

4.1 Rev. A - 03/2022

First issue.


5. Appendix

5.1 Bit and Byte Swapping

DDR3L memories support **bit swapping**, a technique the designer can use to interchange data lines with one another, provided that they correspond to the same byte lane (e.g. any bits inside the D[0..7] lane). This is very useful when trying to optimize a DDR layout routing.


The following figure shows an example of the bit swapping technique which can be implemented in a SAMA5D2 board design.

Figure 5-1. DDR3L Bit Swapping

 

Byte swapping is another technique that can be used on DDR3L memories. It allows the designer to swap the data lanes with one another, also for the purpose of optimizing the layout. Remember to also swap the DQMx and DQSx signals corresponding to the swapped byte lanes, as illustrated below.

Figure 5-2. DDR3L Byte Swapping

 

5.2 Good Practices

The following is a list of suggestions for designing with high-speed signals:

- Use controlled impedance PCB traces that match the specified single-ended (50Ω) and differential (100Ω) impedance.
- Keep the trace lengths of the differential signal pairs as short as possible.
- The differential signal pair traces should be trace-length matched and the maximum trace-length mismatch should not exceed the specified values. Match each differential pair per segment.
- Maintain parallelism and symmetry between differential signals with the trace spacing required to achieve the specified differential impedance.
- Maintain maximum possible separation between the differential pairs, any high-speed clocks/periodic signals (CMOS/TTL) and any connector leaving the PCB (such as I/O connectors, control and signal headers, or power connectors).
- Route differential signals on the signal layer nearest the ground plane using a minimum of vias and corners. This will reduce signal reflections and impedance changes. Use GND stitching vias when changing layers.
- Route CMOS/TTL and differential signals on different layers, which should be isolated by the power and ground planes.
- Avoid tight bends. When it becomes necessary to turn 90° , use two 45° turns or an arc instead of a single 90° turn.
- Do not route traces under crystals, crystal oscillators, clock synthesizers, magnetic devices or ICs that use and/or generate clocks.
- Stubs on differential signals should be avoided due to the fact that stubs will cause signal reflections and affect signal quality.
- Keep the length of high-speed clock and periodic signal traces that run parallel to high-speed signal lines at a minimum to avoid crosstalk. Based on EMI testing experience, the minimum suggested spacing to clock signals is 50 mils.
- Use a minimum of 20 mils spacing between the differential signal pairs and other signal traces for optimal signal quality. This helps to prevent crosstalk.
- Route all traces over continuous planes (VCC or GND), avoiding cross splits or openings in those planes.
- For microstrip or stripline transmission lines, keep the spacing between adjacent signal paths at least twice the line width.
- Keep all traces at least five line widths away from the edge of the board.
- Follow the return path of each signal and keep the width of the return path under each signal path at least as wide, and preferably at least three times as wide, as the signal trace.
- To avoid EMIs, avoid routing switching signals across splits or openings in ground planes. Routing around them is preferable even if it results in longer paths.
- Minimize the loop inductance between the power and ground paths.
- Allocate power and ground planes on adjacent layers with as thin a dielectric as possible to create plane capacitance.
- Route the power and ground planes as close as possible to the surface where the decoupling capacitors are mounted.
- Supply voltages must be composed of planes only, not traces. Short connections (≈ 8 mils) are commonly used to attach vias to planes. Any connections required from supply voltages to vias for device pins or decoupling capacitors should be as short and as wide as possible to minimize trace impedance (20 mils trace width).

The Microchip Website

Microchip provides online support via our website at www.microchip.com/. This website is used to make files and information easily available to customers. Some of the content available includes:

- **Product Support** – Data sheets and errata, application notes and sample programs, design resources, user's guides and hardware support documents, latest software releases and archived software
- **General Technical Support** – Frequently Asked Questions (FAQs), technical support requests, online discussion groups, Microchip design partner program member listing
- **Business of Microchip** – Product selector and ordering guides, latest Microchip press releases, listing of seminars and events, listings of Microchip sales offices, distributors and factory representatives

Product Change Notification Service

Microchip's product change notification service helps keep customers current on Microchip products. Subscribers will receive email notification whenever there are changes, updates, revisions or errata related to a specified product family or development tool of interest.

To register, go to www.microchip.com/pcn and follow the registration instructions.

Customer Support

Users of Microchip products can receive assistance through several channels:

- Distributor or Representative
- Local Sales Office
- Embedded Solutions Engineer (ESE)
- Technical Support

Customers should contact their distributor, representative or ESE for support. Local sales offices are also available to help customers. A listing of sales offices and locations is included in this document.

Technical support is available through the website at: www.microchip.com/support

Microchip Devices Code Protection Feature

Note the following details of the code protection feature on Microchip products:

- Microchip products meet the specifications contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is secure when used in the intended manner, within operating specifications, and under normal conditions.
- Microchip values and aggressively protects its intellectual property rights. Attempts to breach the code protection features of Microchip product is strictly prohibited and may violate the Digital Millennium Copyright Act.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of its code. Code protection does not mean that we are guaranteeing the product is "unbreakable". Code protection is constantly evolving. Microchip is committed to continuously improving the code protection features of our products.

Legal Notice

This publication and the information herein may be used only with Microchip products, including to design, test, and integrate Microchip products with your application. Use of this information in any other manner violates these terms. Information regarding device applications is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. Contact your local Microchip sales office for additional support or, obtain additional support at www.microchip.com/en-us/support/design-help/client-support-services.

THIS INFORMATION IS PROVIDED BY MICROCHIP "AS IS". MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION INCLUDING BUT NOT LIMITED TO ANY IMPLIED WARRANTIES OF NON-INFRINGEMENT, MERCHANTABILITY, AND FITNESS FOR A PARTICULAR PURPOSE, OR WARRANTIES RELATED TO ITS CONDITION, QUALITY, OR PERFORMANCE.

IN NO EVENT WILL MICROCHIP BE LIABLE FOR ANY INDIRECT, SPECIAL, PUNITIVE, INCIDENTAL, OR CONSEQUENTIAL LOSS, DAMAGE, COST, OR EXPENSE OF ANY KIND WHATSOEVER RELATED TO THE INFORMATION OR ITS USE, HOWEVER CAUSED, EVEN IF MICROCHIP HAS BEEN ADVISED OF THE POSSIBILITY OR THE DAMAGES ARE FORESEEABLE. TO THE FULLEST EXTENT ALLOWED BY LAW, MICROCHIP'S TOTAL LIABILITY ON ALL CLAIMS IN ANY WAY RELATED TO THE INFORMATION OR ITS USE WILL NOT EXCEED THE AMOUNT OF FEES, IF ANY, THAT YOU HAVE PAID DIRECTLY TO MICROCHIP FOR THE INFORMATION.

Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights unless otherwise stated.

Trademarks

The Microchip name and logo, the Microchip logo, Adaptec, AnyRate, AVR, AVR logo, AVR Freaks, BesTime, BitCloud, chipKIT, chipKIT logo, CryptoMemory, CryptoRF, dsPIC, FlashFlex, flexPWR, HELDO, IGLOO, JukeBlox, KeeLoq, Kleer, LANCheck, LinkMD, maXStylus, maXTouch, MediaLB, megaAVR, Microsemi, Microsemi logo, MOST, MOST logo, MPLAB, OptoLyzer, PackeTime, PIC, picoPower, PICSTART, PIC32 logo, PolarFire, Prochip Designer, QTouch, SAM-BA, SenGenuity, SpyNIC, SST, SST Logo, SuperFlash, Symmetricom, SyncServer, Tachyon, TimeSource, tinyAVR, UNI/O, Vectron, and XMEGA are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

AgileSwitch, APT, ClockWorks, The Embedded Control Solutions Company, EtherSynch, FlashTec, Hyper Speed Control, HyperLight Load, IntelliMOS, Libero, motorBench, mTouch, Powermite 3, Precision Edge, ProASIC, ProASIC Plus, ProASIC Plus logo, Quiet-Wire, SmartFusion, SyncWorld, Temux, TimeCesium, TimeHub, TimePictra, TimeProvider, WinPath, and ZL are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Adjacent Key Suppression, AKS, Analog-for-the-Digital Age, Any Capacitor, AnyIn, AnyOut, Augmented Switching, BlueSky, BodyCom, CodeGuard, CryptoAuthentication, CryptoAutomotive, CryptoCompanion, CryptoController, dsPICDEM, dsPICDEM.net, Dynamic Average Matching, DAM, ECAN, Espresso T1S, EtherGREEN, IdealBridge, In-Circuit Serial Programming, ICSP, INICnet, Intelligent Paralleling, Inter-Chip Connectivity, JitterBlocker, maxCrypto, maxView, memBrain, Mindi, MiWi, MPASM, MPF, MPLAB Certified logo, MPLIB, MPLINK, MultiTRAK, NetDetach, Omniscient Code Generation, PICDEM, PICDEM.net, PICKit, PICtail, PowerSmart, PureSilicon, QMatrix, REAL ICE, Ripple Blocker, RTAX, RTG4, SAM-ICE, Serial Quad I/O, simpleMAP, SimpliPHY, SmartBuffer, SMART-I.S., storClad, SQL, SuperSwitcher, SuperSwitcher II, Switchtec, SynchroPHY, Total Endurance, TSHARC, USBCheck, VariSense, VectorBlox, VeriPHY, ViewSpan, WiperLock, XpressConnect, and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

The Adaptec logo, Frequency on Demand, Silicon Storage Technology, and Symmcom are registered trademarks of Microchip Technology Inc. in other countries.

GestIC is a registered trademark of Microchip Technology Germany II GmbH & Co. KG, a subsidiary of Microchip Technology Inc., in other countries.

All other trademarks mentioned herein are property of their respective companies.

© 2022, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

ISBN: 978-1-5224-9842-1

AMBA, Arm, Arm7, Arm7TDMI, Arm9, Arm11, Artisan, big.LITTLE, Cordio, CoreLink, CoreSight, Cortex, DesignStart, DynamiQ, Jazelle, Keil, Mali, Mbed, Mbed Enabled, NEON, POP, RealView, SecurCore, Socrates, Thumb, TrustZone, ULINK, ULINK2, ULINK-ME, ULINK-PLUS, ULINKpro, μ Vision, Versatile are trademarks or registered trademarks of Arm Limited (or its subsidiaries) in the US and/or elsewhere.

Quality Management System

For information regarding Microchip's Quality Management Systems, please visit www.microchip.com/quality.

Worldwide Sales and Service

AMERICAS	ASIA/PACIFIC	ASIA/PACIFIC	EUROPE
Corporate Office 2355 West Chandler Blvd. Chandler, AZ 85224-6199 Tel: 480-792-7200 Fax: 480-792-7277 Technical Support: www.microchip.com/support Web Address: www.microchip.com	Australia - Sydney Tel: 61-2-9868-6733 China - Beijing Tel: 86-10-8569-7000 China - Chengdu Tel: 86-28-8665-5511 China - Chongqing Tel: 86-23-8980-9588 China - Dongguan Tel: 86-769-8702-9880 China - Guangzhou Tel: 86-20-8755-8029 China - Hangzhou Tel: 86-571-8792-8115 China - Hong Kong SAR Tel: 852-2943-5100 China - Nanjing Tel: 86-25-8473-2460 China - Qingdao Tel: 86-532-8502-7355 China - Shanghai Tel: 86-21-3326-8000 China - Shenyang Tel: 86-24-2334-2829 China - Shenzhen Tel: 86-755-8864-2200 China - Suzhou Tel: 86-186-6233-1526 China - Wuhan Tel: 86-27-5980-5300 China - Xian Tel: 86-29-8833-7252 China - Xiamen Tel: 86-592-2388138 China - Zhuhai Tel: 86-756-3210040	India - Bangalore Tel: 91-80-3090-4444 India - New Delhi Tel: 91-11-4160-8631 India - Pune Tel: 91-20-4121-0141 Japan - Osaka Tel: 81-6-6152-7160 Japan - Tokyo Tel: 81-3-6880-3770 Korea - Daegu Tel: 82-53-744-4301 Korea - Seoul Tel: 82-2-554-7200 Malaysia - Kuala Lumpur Tel: 60-3-7651-7906 Malaysia - Penang Tel: 60-4-227-8870 Philippines - Manila Tel: 63-2-634-9065 Singapore Tel: 65-6334-8870 Taiwan - Hsin Chu Tel: 886-3-577-8366 Taiwan - Kaohsiung Tel: 886-7-213-7830 Taiwan - Taipei Tel: 886-2-2508-8600 Thailand - Bangkok Tel: 66-2-694-1351 Vietnam - Ho Chi Minh Tel: 84-28-5448-2100	Austria - Wels Tel: 43-7242-2244-39 Fax: 43-7242-2244-393 Denmark - Copenhagen Tel: 45-4485-5910 Fax: 45-4485-2829 Finland - Espoo Tel: 358-9-4520-820 France - Paris Tel: 33-1-69-53-63-20 Fax: 33-1-69-30-90-79 Germany - Garching Tel: 49-8931-9700 Germany - Haan Tel: 49-2129-3766400 Germany - Heilbronn Tel: 49-7131-72400 Germany - Karlsruhe Tel: 49-721-625370 Germany - Munich Tel: 49-89-627-144-0 Fax: 49-89-627-144-44 Germany - Rosenheim Tel: 49-8031-354-560 Israel - Ra'anana Tel: 972-9-744-7705 Italy - Milan Tel: 39-0331-742611 Fax: 39-0331-466781 Italy - Padova Tel: 39-049-7625286 Netherlands - Drunen Tel: 31-416-690399 Fax: 31-416-690340 Norway - Trondheim Tel: 47-72884388 Poland - Warsaw Tel: 48-22-3325737 Romania - Bucharest Tel: 40-21-407-87-50 Spain - Madrid Tel: 34-91-708-08-90 Fax: 34-91-708-08-91 Sweden - Gothenberg Tel: 46-31-704-60-40 Sweden - Stockholm Tel: 46-8-5090-4654 UK - Wokingham Tel: 44-118-921-5800 Fax: 44-118-921-5820