

## Recommended External Circuitry for Transphorm GaN FETs

### Table of Contents

<b>Part I: Introduction.....</b>	<b>2</b>
<b>Part II: Solutions to Suppress Oscillation .....</b>	<b>2</b>
<b>Part III: The di/dt Limits of GaN Switching Devices &amp; Solutions for High-current Operation.....</b>	<b>4</b>
<b>Part IV: Additional Design Notes .....</b>	<b>5</b>

# Application Note 0009

## Part I: Introduction

Transphorm GaN FETs provide significant advantages over silicon (Si) superjunction MOSFETs by offering lower gate charge ( $Q_g$ ), faster switching speeds, and lower body-diode reverse recovery charge ( $Q_{rr}$ ). GaN FETs exhibit in-circuit switching speeds much higher than that of the current Si technologies. The inherent rapid switching of GaN devices reduces current/voltage cross-over power losses, enabling high frequency operation while simultaneously achieving high efficiency.

However, the accompanying high  $di/dt$  transient during switching, combined with parasitic inductances, generates noise voltages in the circuit. This noise can interfere with the gate and the driver of the device, and, in the worst case, creates sustained oscillation that must be prevented for safe operation of the circuit. This application note provides guidance on how to eliminate oscillation and how to achieve high switching current with a controlled  $di/dt$ .

## Part II: Solutions to Suppress Oscillation

To avoid sustained oscillation, it is important to minimize noise generation, to minimize noise feedback, and to damp the ringing energy resulting from the high current/voltage transients. This can be achieved with the recommendations outlined below using a half-bridge switching circuit in Figure 1 as an example.

 



Figure 1. a) Half-bridge switching circuit and b) Efficiency vs. output power

**1) Optimize the PCB layout** to minimize external parasitic inductances and associated feedback. Use a large area ground plane for an overall low-noise base potential. Arrange the gate drive circuit on one side and the output circuit on the other side to minimize noise feedback from the output loop to the input loop. Place the driver circuit close to the gate of the device. Shorten the power loop by arranging the high-side and low-side devices close-by.

**2) Use a gate ferrite bead** [FB1 in Figure 1(a)] to prevent the high-frequency noise from entering the driver and logic circuits. This bead should be mounted close to the Gate lead of the device. NOTE: This is required even for single-ended non-half-bridge designs. The specification of the recommended gate ferrite beads are listed in Transphorm's GaN FET datasheets and also summarized in **Table 2**. The TO247 package includes a built-in gate ferrite bead for our Gen III devices but has been moved to the outside for our latest Gen IV (G4) devices. Please refer to page three of the datasheet to verify its position.


# Application Note 0009

3) Use a DC-link RC snubber [ $RC_{DCL}$  in Figure 1(a)]. The DC rail or DC-link, when decoupled with a low-ESR fast capacitor, can be considered a high-Q C-L network at high frequencies (with "L" being the feed inductance of the DC bus). This can interact with the devices at voltage/current transients and lead to ringing. Adding an RC snubber across the DC-link close to the drain pin of the high-side device can effectively absorb the ringing energy, suppressing potential oscillation. This effect is shown in **Figure 2** where the high-frequency ringing at 25A turn-off is substantially damped with the  $RC_{DCL}$ . Since this snubber is not inserted at the switching node, it does not add switching loss to the circuit. NOTE: This is recommended even for single-ended non-half-bridge designs. The practical values of the  $RC_{DCL}$  can be 2 sets of 6-10Ω/0.5W SMD resistors in series with a 10nF/600-1000V ceramic SMD cap, or 1 set of 3-4Ω/1W resistors in series with a 10-20nF/600-1000V cap if space is limited.

 

**Figure 2. Half-bridge inductive switching waveforms with decoupling capacitor only and with DC-link snubber ( $RC_{DCL}$ ) (Devices: TP65H050WS)**

4) Adding a switching-node RC snubber [ $RC_{SN}$  in Figure 1(a)] can further reduce high-frequency ringing and help control di/dt transients at high operation currents. The effect of the  $RC_{SN}$  on switching waveform at a switching current >50A is shown in **Figure 3**. Unlike the  $RC_{DCL}$ , the capacitance of the  $RC_{SN}$  does increase switching loss. The recommended snubber parameters with little degradation in efficiency are given in the datasheet and are summarized in **Table 2**.

 


**Figure 3. Effect of switching node snubber  $RC_{SN}$  on half-bridge inductive switching waveforms (Devices: TP65H035WS).**

## Part III: The $di/dt$ Limits of GaN Switching Devices & Solutions for High-current Operation

Transphorm GaN FETs are designed for the highest robustness and reliability within the technology boundaries today. These devices can operate to their full voltage rating and at extremely high  $di/dt$  levels in normal operation mode (forward conduction when current enters the Drain). However, when used as a free-wheeling device in reverse conduction mode (current enters the Source when the Gate is off), there are  $di/dt$  limits beyond which the performance can be negatively affected. Although these reverse conduction  $di/dt$  limits in the range of 1200~3800 A/ $\mu$ s (depending on device & stress duration) are much greater than that of typical superjunction devices at ~60A/ $\mu$ s, care must be taken for best performance at high current levels since the  $di/dt$  value is a strong function of switching current.

It is important to note that this  $di/dt$  limit only applies to the device acting as a free-wheeling diode (FWD) and only applies to the duration when the FWD transitions from blocking voltage to reverse conducting current. Three cases are illustrated in **Figure 4**; the affected devices are the ones functioning as an FWD during dead-time when the inductor current commutes from the main switch to the reverse current of the FWD.

- 1) A boost converter that uses an SiC diode as the rectifier device – Not affected.
- 2) A synchronous boost that uses a GaN FET as the FWD –  $Q_2$  affected.
- 3) A synchronous buck that uses a GaN FET as the FWD –  $Q_1$  affected.

 

**Figure 4. Identifying the device affected by the  $di/dt$  limit in three popular circuits: (1) boost converter, (2) synchronous boost converter, and (3) buck converter.**

The maximum  $di/dt$  stress happens when the main switch [ $Q_1$  in **Figure 4** (2) or  $Q_2$  in **Figure 4** (3)] turns off and the inductor current redirects to the FWD instantly. The higher the turn-off current, the higher the reverse conduction  $di/dt$ . The reverse conduction  $di/dt$  limits and associated maximum (turn-off) switching current values are listed in the datasheet. The example for TP65H035WS is shown in **Table 1**. The  $(di/dt)_{RDMC}$  and  $I_{RDMC1}$  values are for constant repetitive switching operation such as in a DC to DC converter, while  $I_{RDMC2}$  applies to DC to AC or AC to DC conversion circuits when the peak current switching is much lower than the average switching current. The  $(di/dt)_{RDMT}$  and  $I_{RDMC}$  values are for transient and continuous transient conditions respectively such as in the event of power-line-disturbance (PLD) in a PFC (when one AC input cycle is missing, which forces the circuit to operate at a much higher current in the next cycle to make up for the energy loss).

# Application Note 0009

Symbol	Parameter	Min	Typ	Max	Unit
$(di/dt)_{RDMC}$	Reverse diode $di/dt$ , repetitive <sup>b</sup>	—	—	1800	A/ $\mu$ s
$I_{RDMC1}$	Reverse diode switching current, repetitive (dc) <sup>c, e</sup>	—	—	28	A
$I_{RDMC2}$	Reverse diode switching current, repetitive (ac) <sup>c, e</sup>	—	—	35	A
$(di/dt)_{RDMT}$	Reverse diode $di/dt$ , transient <sup>d</sup>	—	—	3800	A/ $\mu$ s
$I_{RDMT}$	Reverse diode switching current, transient <sup>d, e</sup>	—	—	45	A

Notes:

- a. Includes dynamic  $R_{DS(on)}$  effect
- b. Continuous switching operation
- c. Definitions: dc = dc-to-dc converter topologies; ac = inverter and PFC topologies, 50-60Hz line frequency
- d.  $\leq 300$  pulses per second for a total duration  $\leq 20$  minutes
- e.  $I_{RDM}$  values can be increased by increasing  $R_G$  and  $RC_{SN}$  on page 3

**Table 1. TP65H035WS reverse diode conduction  $di/dt$  limits and associated max switching current when using the recommended  $R_G$  and  $RC_{SN}$ .**

Note that the reverse diode switching current limits were obtained with the recommended circuit parameters [Figure 1(a) and Table 2]. The gate resistor  $R_G$  is important to control the  $di/dt$  and the addition of a switching node snubber  $RC_{SN}$  offers further improvements when operation current is high. The effect of  $RC_{SN}$  is shown in Figure 1(b): a slight reduction in low-load efficiency, but a significant enhancement at high load. In applications with operation current below 70 percent of the maximum rating or when an  $R_G$  is equal to or higher than the recommended value, the  $RC_{SN}$  can be omitted. On the other hand, one can further increase the  $R_G$  value if the operation current is higher than the maximum  $I_{RDM}$ 's in the datasheet. In all situations, care has to be taken to ensure junction temperature of the devices do not exceed maximum rating.

## Part IV: Additional Design Notes

### 1) Circuit and Layout Recommendations

- As GaN FETs switch extremely fast, we recommend using a driver(s) with sufficient Common Mode Transient Immunity (CMTI) so as not to cause disruption between the secondary and primary side of isolated drivers when in operation.
- When using the GaN FETs in a half bridge configuration, we recommend using an integrated half bridge gate driver(s) that offers overlap protection to prevent outputs VOA and VOB from being high at the same time, such as the Skyworks Si823x series.
- Place the  $RC_{DCL}$  as close as possible to the drain pin of the high-side GaN FET and ground it to the large ground plane.
- SMD mounting is recommended for all snubber components.
- A Gate resistor ( $R_G$ ) is required for all devices.
- Gate ferrite beads (FB1) are only required for TO-220 and PQFN devices; depending on the generation TO-247 devices have built-in ferrite beads (Gen III) where Gen IV (datasheet "G4" designation) use an external ferrite bead. Always review page three of datasheets to get the latest design recommendations.
- If the device is being driven at  $>70$  percent of the rated  $I_{RDM}$  values or a smaller than recommended gate resistor is used, then a switching node RC snubber ( $RC_{SN}$ ) is recommended in addition to the required DC-link RC snubber ( $RC_{DCL}$ ).

# Application Note 0009

- The gate ferrite bead and gate resistor prevent oscillation and reduce excessive  $di/dt$  when the GaN device is used in a half-bridge topology.
- The  $RC_{DCL}$  reduces the voltage ringing due to device interaction with the bypass network.
- The  $RC_{SN}$  slightly reduces light and medium load efficiency with the benefit of increased output power.
- The  $RC_{SN}$  implementation in a half-bridge has the advantage of allowing a higher peak turn-off switching current due to the reduction of the  $di/dt$  seen by the freewheeling device as the main conducting device turns off.

## 2) Required and Recommended External Components for Single Gate Resistor Designs


Device Gate Drive Recommendations for Half Bridge Topologies								
Specifications	GaN FET Devices							
	TP65H015G5WS	TP65H035G4WS/QS	TP65H035WS	TP65H050G4WS/BS/QS	TP65H050WS	TP65H070LDG/LSG	TP65H150G4LSG	TP65H300G4LSG
	TO-247	TO-247/TOLL	TO-247	TO-247/TO-263/TOLL	TO-247	PQFN	PQFN	PQFN
Gate Voltage Drive	0V, 12 V	0V, 12 V	0V, 12V	0V, 12V	0V, 12V	0V, 12V	0V, 12V	0V, 12V
Recommended Gate Resistor ( $R_G$ )	15Ω	30Ω	30Ω	45Ω	45Ω	50-70Ω	60-70Ω	30-60Ω
Recommended Gate Resistor ( $R_G$ ) for 2x to 2.5x $I_{rms}$		47Ω @ 45Apk	47Ω @ 45Apk	47Ω @ 33Apk	47Ω @ 33Apk	TBD	TBD	TBD
Topology: AC to DC or DC to AC								
DC Link Snubber ( $RC_{DCL}$ )	[10pF, 3.3Ω] x 3	[4.7nF, 5Ω] x 2	[10nF, 8Ω] x 2	[4.7nF, 8Ω] x 2	[10nF, 8Ω] x 2	[10nF, 10Ω] x 2	[4.7 - 10nF, 5Ω]	[4.7 - 10nF, 5Ω]
Ferrite Bead Gate (FB1) @ 100 MHz	80-120Ω	200-270Ω	Internal	200-300Ω	Internal	240Ω	240Ω	240Ω
Recommended $RC_{SN}$	[100pF, 10Ω] x 3	[100pF, 10Ω]	[200pF, 5Ω]	[200pF, 5Ω]	[100pF, 10Ω]	[68pF, 15Ω]	[22pF, 15Ω]	[22pF, 15Ω]
Datasheet Specification di/dt Maximums								
Specifications	GaN FET Devices							
	TP65H015G5WS	TP65H035G4WS	TP65H035WS	TP65H050G4WS/BS	TP65H050WS	TP65H070LDG/LSG	TP65H150G4LSG	TP65H300G4LSG
	TO-247	TO-247	TO-247	TO-247/TO-263	TO-247	PQFN	PQFN	PQFN
Reverse diode max (di/dt), repetitive (A/μs) - di/dt <sub>EDMC</sub>	3500	3200	1800	2500	1600	1200	1200	1200
Reverse diode max switching current, dc-dc repetitive (A) - $I_{RDMC1}$	--	--	28	--	24	18	--	--
Reverse diode max switching current, ac repetitive (A) - $I_{RDMC2}$	--	--	35	--	28	23	--	--
Reverse diode max (di/dt), transient (A/μs) - di/dt <sub>EDMT</sub>	--	--	3800	--	3000	2600	--	--
Reverse diode max switching current, transient (A) - $I_{RDMT}$	--	--	45	--	36	28	--	--

**Table 2. Recommended components for half-bridge circuit in Figure 1(a).**

### 3) To Verify GaN FET Stable Operation

To verify adequate operational margin without oscillation, as a minimum observe the  $V_{DS}$  waveforms at the turn-on and turn-off switching edges at the application's maximum drain current. This may occur during start-up or at the application's maximum load step. A double-pulse or multi-pulse test is highly recommended utilizing the actual layout, with current levels at or greater than 120 percent of the application's anticipated peak current. Verify that the ringing on the  $V_{DS}$  waveform at the transition edges is adequately damped. See design guide [DG004: Multi-pulse Testing for GaN Layout Verification](#).

4) Recommended Driving Gate Resistance using a single  $R_G$  or dual  $R_{G(on)}$  and  $R_{G(off)}$

 

**Figure 5. Driving circuits: (a) Single output driver with a single  $R_g$ ,  
(b) single output driver with different turn-on and turn-off  $R_g$ , and (c) dual output driver with different turn-on and turn-off  $R_g$ .**

# Application Note 0009

The driver circuits with different configurations of driver and gate resistor are shown in Figure 5. A proper gate resistor is effective to limit the switching  $di/dt$  and keep the switching stable. As described in part III, the  $di/dt$  limit only applies to the device acting as a free-wheeling diode (FWD), i.e. the turn-off switching speed of the active device should be controlled, and only large turn-off  $R_g$  should be chosen but turn-on  $R_g$  can be small to reduce the turn-on power loss. The separate turn-on and turn-off  $R_g$  can be achieved using a Schottky diode in series with a  $R_{g1}$  resistor paralleling with a  $R_{g2}$  resistor, as shown in Figure 5 (b). It should be noticed that the direction of diode is different from that in the gate driving circuit of Si MOSFET. The equivalent turn-on  $R_{g\_on}$  is  $R_{g1} \cdot R_{g2} / (R_{g1} + R_{g2})$ , and turn-off  $R_g$  value is same with  $R_{g2}$ . It is convenient to configure the turn-on and turn-off  $R_g$  when a dual output driver IC is used, as shown in Figure 5 (c). Although there is no  $di/dt$  limit for turn-on, a proper turn-on  $R_g$  should be carefully selected to avoid cross-talk issues in high-speed switching half bridge circuit using 3 pin TO-220 and TO-247 packaged devices. The recommended equivalent gate resistor values for different GaN devices are listed in Table 3. For improving noise immunity during turn-off, a -3V gate drive voltage can be considered but the turn off  $R_g$  should be increased to maintain the same  $di/dt$  and turn-on  $R_g$  can be reduced to keep same turn-on switching speed.

Device Gate Drive Recommendations for Half Bridge Topologies							
Specifications	GaN FET Devices						
	TP65H015G5WS	TP65H035G4WS/QS	TP65H035WS	TP65H050G4WS/BS/QS	TP65H050WS/QS	TP65H070LDG/LSG	TP65H150G4PS/LSG
	TO-247	TO-247/TOLL	TO-247	TO-247/TO-263/TOLL	TO-247	PQFN	TO-220/PQFN
Gate Voltage Drive	0V, 12 V	0V, 12 V	0V, 12V	0V, 12V	0V, 12V	0V, 12V	0V, 12V
Recommended Gate Resistor $R_{G(on)}$	5Ω	22Ω	30Ω	30Ω	33Ω	33Ω	22 to 30Ω
Recommended Gate Resistor $R_{G(off)}$	15Ω	47Ω	47Ω	47Ω	47Ω	47 to 56Ω	33 to 47 Ω
Recommended Gate Resistor ( $R_g$ ) for 2x to 2.5x $I_{rms}$ Topology: AC to DC or DC to AC	TBD	47Ω @ 45Apk	47Ω @ 45Apk	47Ω @ 33Apk	47Ω @ 33Apk	TBD	TBD
Gate Voltage Drive	-3V, 12 V	-3V, 12 V	-3V, 12 V	-3V, 12 V	-3V, 12 V	-3V, 12 V	-3V, 12 V
Recommended Gate Resistor $R_{G(on)}$	15Ω	18Ω	25 to 30Ω	25 to 30Ω	25 to 30Ω	22 to 30Ω	18-25Ω
Recommended Gate Resistor $R_{G(off)}$	TBD	47Ω to 56Ω	47 to 56Ω	47 to 56Ω	47 to 56Ω	47 to 56Ω	33 to 47Ω