

Generating USB Type-C (also called USB-C) charging power for multiple peripherals requires a flexible DC/DC converter that can work with a controller to deliver the desired voltage and current capability to the corresponding device. As power density increases — particularly in multiple-power port or hub applications — efficiency becomes paramount, and requires the lowest power loss to minimize internal heat. The programmable power supply (PPS) specification for USB power sourcing adds even more functionality for the power conversion device to integrate.

This article will focus on how to implement a complete USB C power delivery (PD) solution with flexible functionality. The system must meet the demands of the current and voltage regulations listed in the PPS specifications, while still enabling fully functional USB Type-C products. It will cover the major aspects of design, including component selection, board layout, and functional optimization using programmable features and settings. Using the MPQ4272 boost / buck converter and [MPQ4230](#) buck-boost converter from MPS as examples, device operation will be analyzed to optimize the switching frequency and peak current to minimize power delivery losses. This article will also describe how to utilize a DC/DC converter with a suitable USB PD controller for a complete PD solution.

The USB Programmable Power Supply (PPS) Specification Requirements

The PPS standard is part of the USB PD Specification (available at [usb.org](#)), and mainly focuses on facilitating fast battery charging. A PPS power source can exchange data with the powered device every 10 seconds, so the power source can dynamically adjust the output voltage and current according to the conditions set by the device that is receiving the USB power. PPS capabilities allow for small stepwise changes to be made to the voltage and current. The receiving powered device can request that the source make these changes. This power source control is an effective way to reduce power conversion losses, which is especially useful when a dedicated battery charger adds another level of conversion loss.

The standard process for charging a Lithium-ion battery starts with a constant current charging state (maintaining a fixed constant current while the battery voltage gradually increases). Then after reaching a specific voltage, the charging changes to constant voltage (maintaining a fixed voltage while the charge current gradually reduces). Figure 1 shows the charging profile of a Li-ion battery.

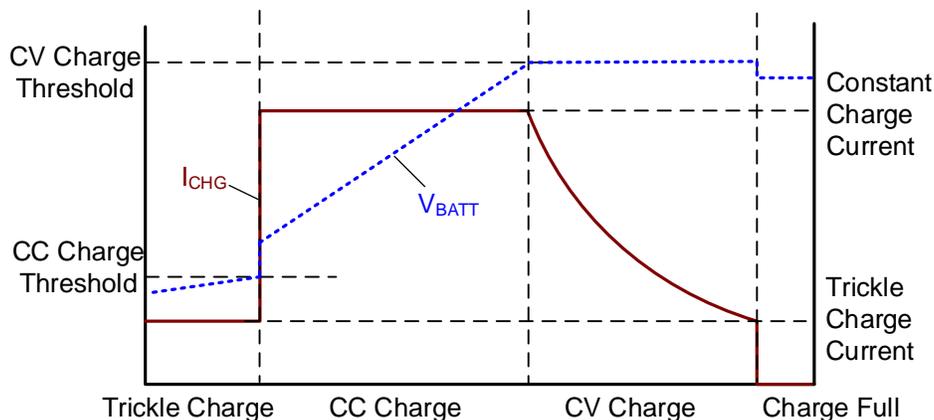


Figure 1: Lithium-Ion Charging Profile

Earlier USB specifications allowed for a fixed 5V supply voltage. USB C PD specifications have evolved to include other higher-voltage options, but did not include a stepped voltage variation. The main method to charge batteries required a buck regulator-charger, which added another conversion step that generated heat and reduced efficiency.

The PPS standard allows the USB C power source to provide voltage and current control for direct battery charging and to reduce the power losses. The nominal step sizes for a PPS power source are 20mV for output voltage and 50mA for current limiting. The voltage range includes a 3.3V minimum and a 21V maximum. These ranges, coupled with USB communications protocol, enable an intelligent charging solution for single- or multi-cell battery supplies. The incremental voltage control also addresses applications where cable losses to powered devices require compensation for the I-R voltage drop to the load.

USB Power Source Solutions

The output for a USB Type-C source must adhere to output voltage and current specifications. The input for the source, however, can have a variety of characteristics, such as a wide or narrow voltage range, and low to high power capabilities. Selecting a power conversion device for the power source requires taking that input source into consideration, along with the desired output capabilities, such as full USB Type-C and PPS functions.

Since the maximum output voltage from the source is 21V, a power source exceeding 21V requires the use of a buck DC/DC converter (also called step-down converter). Many applications are limited to a lower voltage, such as automotive 12V batteries, which require using a buck-boost DC/DC converter to convert an input voltage for both higher and lower output voltages. Buck converters are normally more cost-effective due to having just two power switches versus the buck-boost with four, although buck-boost converters are much more versatile. Both of these solutions will be explored in this article (see Figure 2).

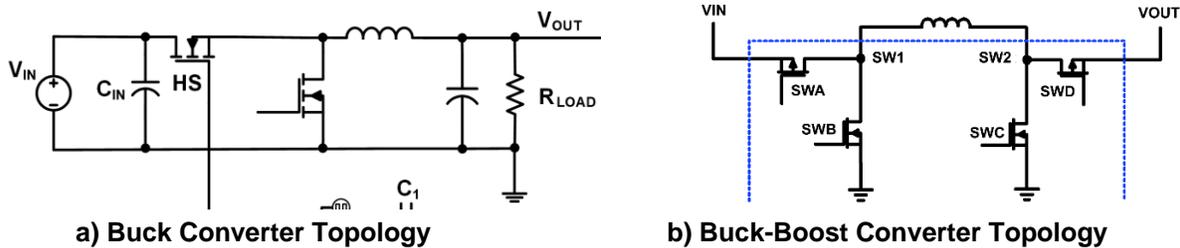


Figure 2: USB Power Source Solutions

A complete USB Type-C solution needs a power conversion component and a USB PD controller. The controller performs the necessary handshaking with the receiving power sink device, then communicates the proper set-up information to the DC/DC converter to ensure that power is delivered to the USB port. An example utilizing a DC/DC converter with a controller is discussed below.

USB Type-C Buck Converter Solution

An ideal USB C buck converter solution would include high-efficiency, synchronous switching FETs, a versatile control element with built-in compensation, and a serial communications interface that provides a direct link to the USB controller device. Some devices, such as the MPQ4272 from MPS, provide these functions with a dual-output configuration for dual-port USB applications. We’ll explore this specific part as an example for buck USB Type-C solutions. The MPQ4272 buck converter offers a maximum 36V input voltage, and load currents up to 3A at each output, yielding a dual-output, 60W supply solution (see Figure 3).

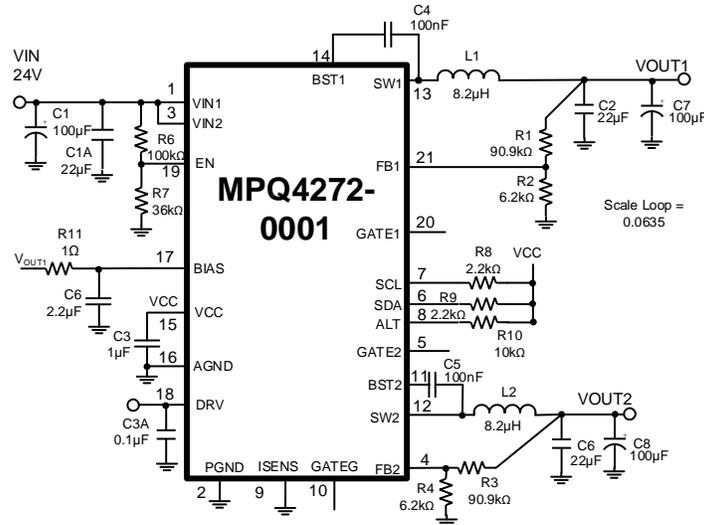


Figure 3: $V_{IN} = 24V$, V_{OUT1} , $V_{OUT2} = 3.3V$ to $21V$, $3A$ Load

Figure 3 shows a circuit that utilizes a 24V input from an AC/DC wall adapter, and converts to two outputs capable of a 3.3V to 21V range suitable for PPS. The SCL and SDA signals are the I²C serial interface that access registers for general control, as well as current and voltage control. Telemetry is provided with voltage-, current-, and temperature-monitoring functions.

Solution features include line drop compensation for improved USB output voltage regulation, selectable switching frequency, and up to 98% efficiency (see Figure 4). This high efficiency is mainly due to the power MOSFET $R_{DS(ON)}$ values of 22mΩ on the high side and 26mΩ on the low side, which yield very low power dissipation and a case temperature rise of only 40°C with both channels powering 5V, 3A loads (recommended layout on 4-layer PCB).

Efficiency vs. Load Current

$V_{IN} = 24V$, $f_{SW} = 420kHz$, PWM mode,
buck 1 = buck 2, $I_{O1} = I_{O2}$

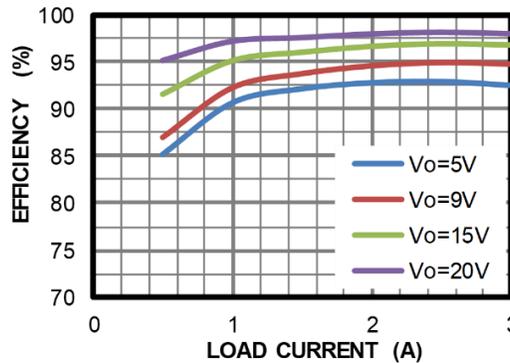


Figure 4: MPQ4272 Efficiency Curve

The output voltage control has adjustable step size and can easily meet 20mV per step, and a constant current control mode with 50mA steps, which is required for PPS operation.

Buck-Boost USB Type-C Solution

USB Type-C power products that use other lower power sources — such as a 12V wall adapter or a device with varying input sources — need both buck and boost DC/DC modes to produce the full 3.3V to 21V output voltage range.

The [MPQ4230](#) is a buck-boost solution with a maximum 36V input voltage and four integrated switching MOSFETs to support single-inductor buck-boost conversion. It is capable of a 3A load current for a 20V output, with inputs as low as 9V. As one example of an optimal solution, the MPQ4230 can cleanly handle switching in either buck or boost mode via the control circuitry. When the input supply voltage is close to the regulated output voltage, a special buck-boost mode is engaged, whereby all four switches are sequenced to provide effective power transfer to the load. Output constant current and voltage control includes proper step sizes for PPS operation.

Figure 5 shows the MPQ4230 powering a single USB Type-C port with USB-PD and PPS capabilities. The MPQ4230’s regulated output voltage is connected directly to the MPQ5031’s USB VBUS signal. The PD controller is the MPQ5031, a downstream-facing port (DFP) for USB provider applications. It uses the I²C serial interface to control the MPQ4230’s operation, including enabling the device, setting the output voltage and current limit, and adjusting parameters such as line drop compensation.

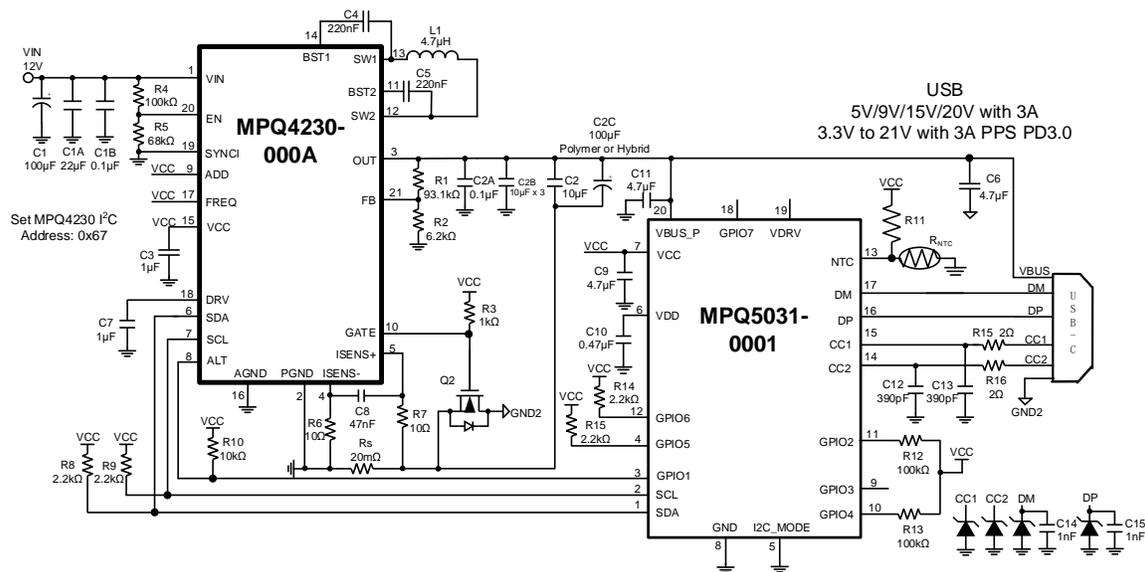


Figure 5: $V_{IN} = 12V$, $V_{OUT} = 3.3V$ to $21V$ for USB PD and PPS Applications

Conclusion

USB single- and multi-port power products are now available with extended functionality for better control across many applications, including direct battery charging with PPS functions. Devices and solutions were presented for powering USB Type-C ports that require USB-PD and PPS functionality, which is becoming increasingly common in the latest consumer and automotive products for a variety of applications. High efficiency, full protection features, and versatile programmable functions in these types of solutions yield high-performance, cost-effective power delivery.